

AC Bridges

Introduction

Measurement of Self Inductance

Measurement of Capacitance

Measurement of Frequency

Measurement of Medium Resistance

Fundamental

AC bridges are applied to measure inductance, capacitance, storage factor and loss factor of active elements of an ac circuit. This type of bridges are also used for phase shifting, to provide feedback path for oscillators and amplifiers, to filter out unwanted signals.

Sources: The source used in ac bridges is power line for measuring at low frequencies in addition to electronic oscillators for measuring at high frequencies.

Detectors: Headphones, Vibration Galvanometer and Tunable amplifiers are commonly used as detectors in ac bridges.

General Equation of AC Bridge

An AC bridge is shown in figure (1). At balance,

$$E_1 = E_2 \Rightarrow I_1 Z_1 = I_2 Z_2 \quad (1)$$

Similarly, at balance condition the current

$$I_1 = I_3 = \frac{E}{Z_1 + Z_3}, \quad I_2 = I_4 = \frac{E}{Z_2 + Z_4} \quad (2)$$

Using equation (1) and (2)

$$\frac{E}{Z_1 + Z_3} \cdot Z_1 = \frac{E}{Z_2 + Z_4} \cdot Z_2 \quad (3)$$

$$\Rightarrow Z_1 Z_4 = Z_2 Z_3 \quad (4)$$

$$\Rightarrow Y_1 Y_4 = Y_2 Y_3 \quad (5)$$

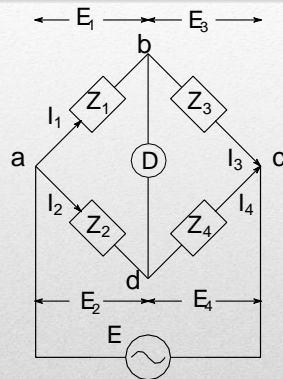


Figure 1: AC bridge

General Equation of AC Bridge

From equation (4), the polar form of balance equations are

$$Z_1 < \theta_1, Z_4 < \theta_4 = Z_2 < \theta_2, Z_3 < \theta_3 \quad (6)$$

$$\Rightarrow Z_1 Z_4 < (\theta_1 + \theta_4) = Z_2 Z_3 < (\theta_2 + \theta_3) \quad (7)$$

If $Z_1 = R_1 + jX_1$, $Z_2 = R_2 + jX_2$, $Z_3 = R_3 + jX_3$ and $Z_4 = R_4 + jX_4$ then, using equation (4)

$$(R_1 + jX_1)(R_4 + jX_4) = (R_2 + jX_2)(R_3 + jX_3) \quad (8)$$

$$R_1 R_4 - X_1 X_4 + j(R_1 X_4 + R_4 X_1) = R_2 R_3 - X_2 X_3 + j(R_2 X_3 + R_3 X_2) \quad (9)$$

Equating real and imaginary part of equation (9), the balance equations

$$R_1 R_4 - X_1 X_4 = R_2 R_3 - X_2 X_3 \quad (10)$$

$$R_1 X_4 + R_4 X_1 = R_2 X_3 + R_3 X_2 \quad (11)$$

General Equation of AC Bridge

As shown in figure (2) and by using balance equation (4)

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) R_4 = (R_2 + j\omega L_2) R_3$$

$$R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega L_2 R_3 \quad (12)$$

Equating real and imaginary part of equation (12)

$$R_1 = R_2 R_3 / R_4 \quad (13)$$

$$L_1 = L_2 R_3 / R_4 \quad (14)$$

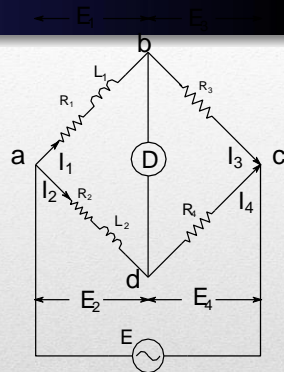


Figure 2: AC bridge

Maxwell's Inductance-Capacitance Bridge

Here,

L_1 = unknown inductance, R_1 = effective resistance of L_1 , R_2 , R_3 , R_4 = non-inductive resistances, C_4 = variable standard capacitor.

At balance,

$$(R_1 + j\omega L_1) \cdot \frac{R_4}{1 + j\omega C_4 R_4} = R_2 R_3 \quad (15)$$

$$R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega R_2 R_3 R_4 C_4 \quad (16)$$

Equating real and imaginary part of equation (16)

$$R_1 = R_2 R_3 / R_4 \quad (17)$$

$$L_1 = R_2 R_3 C_4 \quad (18)$$

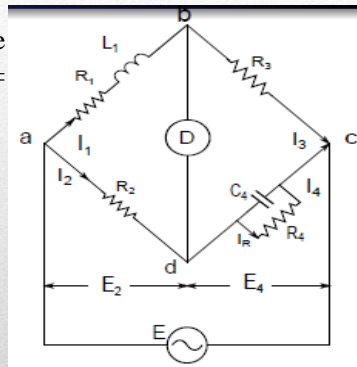


Figure 3: Maxwell's AC Bridge

Maxwell's Inductance-Capacitance Bridge

Q factor of the coil,

$$Q = \frac{\omega L_1}{R_1} = \omega R_4 C_4 \quad (19)$$

Advantages:

- i) Two balance equations are independent if R_4 and C_4 are chosen as variable
- ii) Independent of frequency
- iii) Simple expression of R_1 and L_1
- iv) Useful for wide range measurement

Disadvantages:

- i) Expensive variable capacitor
- ii) Low Q factor (around $1 < Q < 10$)

Hay's Bridge

L_1 =Unknown inductance with resistance R_1 R_2 , R_3 ,

R_4 = Known non-inductive resistance

C_4 = Standard capacitance

At balance condition of the bridge,

$$(R_1 + j\omega L_1)(R_4 - j/\omega C_4) = R_2 R_3 \quad (20)$$

$$R_1 R_4 + \frac{L_1}{C_4} + j\omega L_1 R_4 - \frac{jR_1}{\omega C_4} = R_2 R_3 \quad (21)$$

Equating real and imaginary part of equation (21)

$$R_1 R_4 + L_1 / C_4 = R_2 R_3 \quad (22)$$

$$L_1 = \frac{R_1}{\omega^2 R_4 C_4} \quad (23)$$

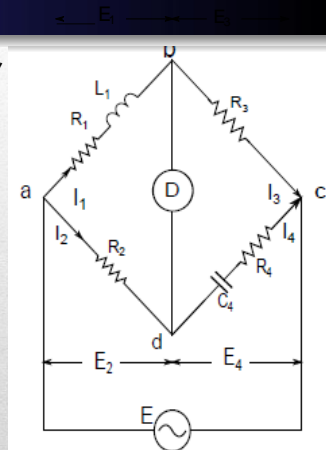


Figure 4: Hay's Bridge

Hay's Bridge

Solving equation (22) yields

$$L_1 = \frac{R_2 R_3 C_4}{1 + \omega^2 C_4^2 R_4^2} \qquad R_1 = \frac{\omega^2 R_2 R_3 R_4 C_4^2}{1 + \omega^2 C_4^2 R_4^2} \quad (24)$$

Q factor of the coil,

$$Q = \frac{\omega L_1}{R_1} = 1/\omega C_4 R_4 \quad (25)$$

The expression of L_1 is dependent of frequency. In terms of Q , L_1 can be re-expressed as

$$L_1 = \frac{R_2 R_3 C_4}{1 + (1/Q)^2} \quad (26)$$

For high value of Q , the frequency dependency can be neglected, and hence $L_1 \approx R_2 R_3 C_4$ which is same as Maxwell's inductance capacitance bridge

Hay's Bridge

Advantages:

- i) Simple expression of Q and unknown inductance for high $Q > 10$
- ii) Requires only low value of R_4 for high Q

Disadvantages:

- iii) Expensive variable capacitor
- iv) Not suitable for low value of $Q < 10$

Anderson's Bridge

L_1 = Self inductance to be measured

r_1 = Resistance of L_1

R_1 = Resistance connected in series with L_1

r, R_2, R_3, R_4 non-inductive resistances

C = fixed standard capacitor.


At balance

$$I_1 = I_3$$

$$I_2 = I_4 + I_c$$

and
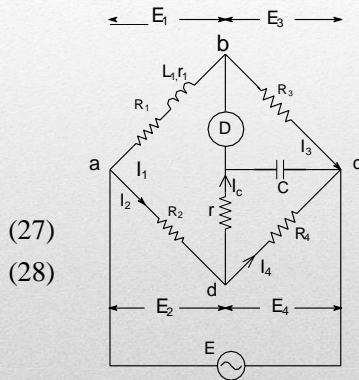
$$I_1 R_3 = I_c \frac{1}{j\omega C} \Rightarrow I_c = jI_1 \omega C R_3$$



(29) Figure 5: Anderson's ac bridge

Anderson's Bridge

Another balance equations

$$E_1 = E_2 + I_c r \quad (30)$$

$$I_c \left(r + \frac{1}{j\omega C} \right) = (I_2 - I_c) R_4 \quad (31)$$

From equation (30),

$$I_1(R_1 + r_1 + j\omega L_1) = I_2 R_2 + I_c r \quad (32)$$

$$\Rightarrow I_1(R_1 + r_1 + j\omega L_1 - j\omega C R_3 r) = I_2 R_2 \quad (33)$$

and from equation (31)

$$j I_1 \omega C R_3 \left(r + \frac{1}{j\omega C} \right) = (I_2 - j I_1 \omega C R_3) R_4 \quad (34)$$

$$\Rightarrow I_2 = \frac{R_3}{R_4} I_1 + \frac{j\omega C R_3 r}{R_4} I_1 + j\omega C R_3 I_1 \quad (35)$$

Anderson's Bridge

Using the value of I_2 from equation (35) in equation (33) results

$$I_1(R_1 + r_1 + j\omega L_1 - j\omega CR_3r) = I_1 \left[\frac{R_3}{R_4} + \frac{j\omega CR_3r}{R_4} + j\omega CR_3 \right] R_2 \quad (36)$$

$$\Rightarrow (r_1 + R_1) + j(\omega L_1 - \omega CR_3r) = \left[\frac{R_2R_3}{R_4} + j \frac{\omega CR_2R_3r}{R_4} + \omega CR_2R_3 \right] \quad (37)$$

Equating real part of equation (37)

$$r_1 + R_1 = \frac{R_2R_3}{R_4} \Rightarrow r_1 = \frac{R_2R_3}{R_4} - R_1 \quad (38)$$

similarly, equating imaginary part of equation (37)

$$\omega L_1 - \omega CR_3r = \frac{\omega CR_2R_3r}{R_4} + \omega CR_2R_3 \quad (39)$$

$$\Rightarrow L_1 = C \frac{R_3}{R_4} [r(R_2 + R_4) + R_2R_4] \quad (40)$$

Anderson's Bridge

Advantages:

- i) r_1 and r are independent
- ii) Fixed capacitor
- iii) May be used for accurate determination of capacitance in terms of inductance

Disadvantages:

- i) Bridge is complex
- ii) Additional junction points increase the difficulty of shielding the bridge

This method is capable of precise measurements of inductances over a wide range of values from a few micro-henrys to several henrys and is one of the commonest and the best bridge methods.

De-Sauty Bridge

Consider figure (6)(a) where,

C_1 = Capacitor whose capacitance to be measured

C_2 = Standard capacitor

R_1 = resistance connected in series with C_1

R_2, R_4 = non-inductive resistances

At balance

$$Z_1 Z_4 = Z_2 Z_3 \quad (41)$$

$$\Rightarrow \frac{1}{j\omega C_1} \cdot R_4 = \frac{1}{j\omega C_2} \cdot R_3 \quad (42)$$

$$\Rightarrow C_1 = C_2 \cdot \frac{R_4}{R_3} \quad (43)$$

Though the circuit is simple, it is used only for loss-less capacitor.

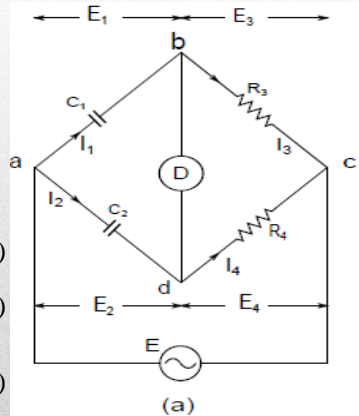


Figure 6: De-Sauty ac bridge

Modified De-Sauty Bridge

The bridge is modified then by De-Sauty as shown in figure (7) where, r_1 and r_2 are the loss component of capacitor C_1 and C_2 respectively.

Here, at balance condition

$$Z_1 Z_4 = Z_2 Z_3 \quad (44)$$

$$(R_1 + r_1 - j \frac{1}{\omega C_1}) R_4 = (R_2 + r_2 - j \frac{1}{\omega C_2}) R_3 \quad (45)$$

Equating the imaginary and real part of equation (45) results

$$\frac{R_4}{\omega C_1} = \frac{R_3}{\omega C_2} \Rightarrow \frac{C_1}{C_2} = \frac{R_4}{R_3} \quad (46)$$

$$(R_1 + r_1) R_4 = (R_2 + r_2) R_3 \Rightarrow \frac{R_2 + r_2}{R_1 + r_1} = \frac{R_4}{R_3} \quad (47)$$

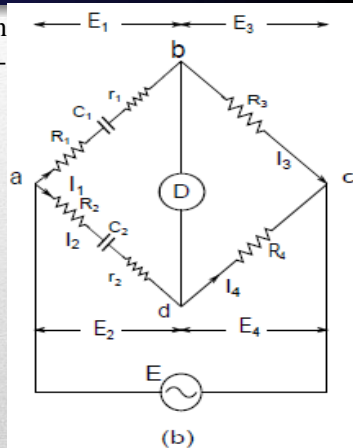


Figure 7: Modified De-Sauty bridge

Modified De-Sauty Bridge

By using equations (46) and (47)

$$\frac{C_1}{C_2} = \frac{R_2 + r_2}{R_1 + r_1} = \frac{R_4}{R_3} \quad (48)$$

Dissipation factor of the capacitor

$$C_1 : D_1 = \omega C_1 r_1 \quad C_2 : D_2 = \omega C_2 r_2$$

From equation (48) it can be written that

$$\begin{aligned} C_2 r_2 - C_1 r_1 &= C_1 R_1 - C_2 R_2 \Rightarrow \omega C_2 r_2 - \omega C_1 r_1 = \omega (C_1 R_1 - C_2 R_2) \\ \Rightarrow D_2 - D_1 &= \omega (C_1 R_1 - C_2 R_2) \\ \Rightarrow D_2 - D_1 &= \omega C_2 \left(\frac{R_1 R_4}{R_3} - R_2 \right) \end{aligned} \quad (49)$$

Therefore, dissipation factor of one capacitor can be obtained if it is known of other. However, due to difference between $\frac{R_1 R_4}{R_3}$ and R_2 , this method does not give accurate measurement of dissipation factor.

Schering Bridge

C_1 = Capacitor whose capacitance to be measured

r_1 = loss component of C_1

C_2 = Standard capacitor

R_3 = Standard non-inductive resistor

R_4 = non-inductive variable resistor

C_2 = standard variable capacitor

At balance condition

$$Z_1 Z_4 = Z_2 Z_3 \quad (50)$$

$$\Rightarrow \left(r_1 + \frac{1}{j\omega C_1} \right) \frac{R_4}{1 + j\omega C_4 R_4} = \frac{1}{j\omega C_2} R_3$$

$$\Rightarrow r_1 R_4 - j \frac{R_4}{\omega C_1} = -j \frac{R_3}{\omega C_2} + \frac{R_3 R_4 C_4}{C_2} \quad (51)$$

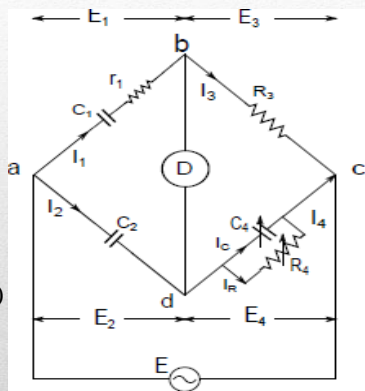


Figure 8: Schering AC bridge

Schering Bridge

Equating real part of equation (51),

$$r_1 R_4 = \frac{R_3 R_4 C_4}{C_2} \Rightarrow r_1 = \frac{R_3 C_4}{C_2} \quad (52)$$

Equating imaginary part of equation (51),

$$\frac{R_4}{\omega C_1} = \frac{R_3}{\omega C_2} \Rightarrow C_1 = C_2 \frac{R_4}{R_3} \quad (53)$$

So, the value of r_1 and C_1 can be obtained independently if R_4 and C_4 are variable.

Dissipation factor:

$$D = \omega C_1 r_1 = \omega C_2 \frac{R_4}{R_3} \frac{R_3 C_4}{C_2} = \omega C_4 R_4 \quad (54)$$

Wien's Bridge

The most important bridge to determine frequency in terms of various bridge elements is Wien bridge as shown in figure (9) that is describe below. This bridge can be used as notch filter as well as audio and RF oscillators.

At balance condition,

$$\frac{R_1}{1 + j\omega C_1 R_1} R_4 = R_2 - \frac{j}{\omega C_2} R_3 \quad (55)$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} + \frac{C_1}{C_2} + j \omega C_1 R_2 - \frac{1}{\omega C_2 R_1} \quad (56)$$

Equating real part yields

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} + \frac{C_1}{C_2} \quad (57)$$

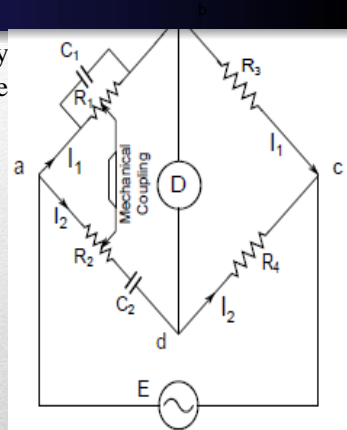


Figure 9:Wien's bridge

Wien's Bridge

Equating imaginary part yields

$$\omega C_1 R_2 - \frac{1}{\omega C_2 R_1} = 0 \Rightarrow \omega = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{R_1 R_2 C_1 C_2}} \quad (58)$$

In most Wien's bridge, the components are so chosen that $R_1 = R_2 = R$ and $C_1 = C_2 = C$. Therefore, the frequency becomes,

$$f = \frac{1}{2\pi RC} \quad (59)$$

Campbell's bridges is self study and Assignment

Limitations of Wheatstone Bridge

Wheatstone bridge is not suitable for low and high resistance due to the following reasons:

- It can measure from few Ω to several $M\Omega$.
- Upper limit is set by reducing the sensitivity to unbalance caused by resistance values.
- Upper limit can be extended by increasing EMF that causes heat
 - inaccuracy due to leakage out of insulation.
- Contact resistance presents a source of uncertainty that is difficult to overcome.

Precision Measurement of Medium Resistance

- In case of medium resistance measurements with Wheatstone bridge, the following factors should be taken into consideration:
- Resistance of connecting wire leads to Thermoelectric effects and Temperature effects.
- Contact resistances
- In precision measurements, the accurate comparisons are made on an equal ratio bridge with a fixed standard nominally equal to the resistance under test. The problem is further reduced by determining the exact ratio of R to S or the difference between them.

Carey Foster Slide Wire Bridge

Resistance P and Q are adjusted so that the ratio P/Q is approximately equal to the ratio R/S . Let, balanced point d is obtained at a distance l_1 as shown in

Figure below.

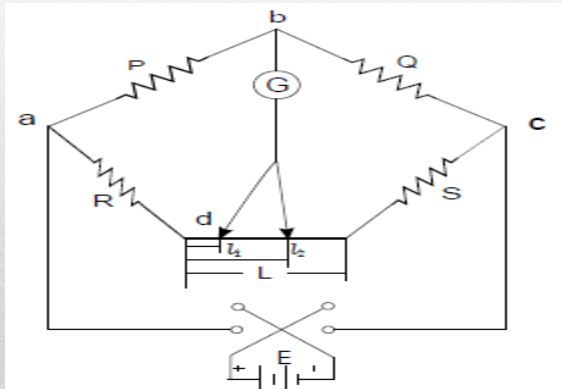


Figure : Carey Foster bridge to measure medium resistance

Carey Foster Slide Wire Bridge

Therefore at balance condition,

$$\frac{P}{Q} = \frac{R + l_1 r}{S + (L - l_1)r} \quad (34)$$

$$\frac{P}{Q} + 1 = \frac{R + l_1 r + S + (L - l_1)r}{S + (L - l_1)r} = \frac{R + S + Lr}{S + (L - l_1)r} \quad (35)$$

where, r is the resistance per unit length of the slide wire. Then R and S are interchanged and balanced obtained again at a distance l_2 . Similarly for second balance point,

$$\frac{P}{Q} = \frac{S + l_2 r}{R + (L - l_2)r} \quad (36)$$

$$\frac{P}{Q} + 1 = \frac{S + l_2 r + R + (L - l_2)r}{R + (L - l_2)r} = \frac{R + S + Lr}{R + (L - l_2)r} \quad (37)$$

Carey Foster Slide Wire Bridge

From equation (35) and (37)

$$S + (L - l_1)r = R + (L - l_2)r \quad (38)$$

$$S - R = (l_1 - l_2)r \quad (39)$$

Thus the difference between S and R is obtained from the resistance per unit length of the slide wire and the difference $(l_1 - l_2)$ between the two slide wire lengths at balance.

The slide wire is calibrated, i.e. r is obtained by shunting either S or R by a known resistance and again determining the difference in length $(l'_1 - l'_2)$.

Suppose, S is known and S' is its value when shunted by unknown resistance.

Carey Foster Slide Wire Bridge

After shunting S equation (39) becomes

$$S' - R = (l'_1 - l'_2)r \quad (40)$$

Therefore, equation (39) and (40) yield

$$\frac{S - R}{l_1 - l_2} = \frac{S' - R}{l'_1 - l'_2} \quad (41)$$

$$R = \frac{S(l'_1 - l'_2) - S'(l_1 - l_2)}{l'_1 - l'_2 - l_1 + l_2} \quad (42)$$

The equation (42) shows that this method gives the direct comparison between R and S in terms of length only and the Resistances of P and Q contact, and the Resistances of connecting leads are eliminated.